

Experiment 2

Hand Calculations


(262538)

Shane Reynolds.

The circuit given in this practical can be divided into two main components:

- A current source in the form of a current mirror.
- An active loaded Differential Amp.

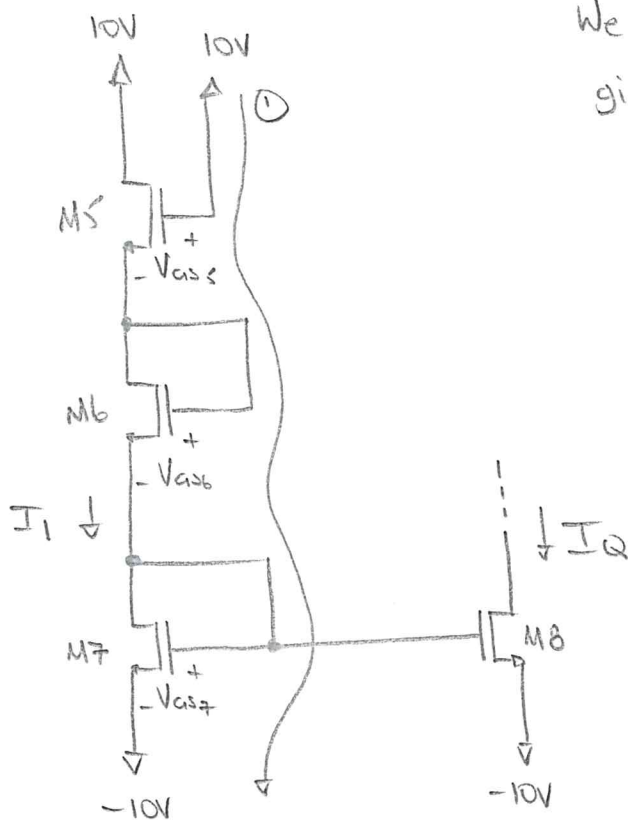Consider the current source component shown below:



We want to find I_1 given:

$$k_{n5} = k_{n6} = 50 \mu\text{A}/\text{V}^2$$

$$k_{n7} = 200 \mu\text{A}/\text{V}^2$$

$$\lambda = 0.01 \text{ V}^{-1}$$

if we take a KVL by loop

①:

$$-10 + V_{GS5} + V_{GS6} + V_{GS7} - 10 = 0.$$

Since M_5 & M_6 are identical

$$\therefore 2V_{GS6} + V_{GS7} = 20. \quad -1)$$

Now, assuming M_5 , M_6 & M_7 are operating in saturation:

$$I_{D5} = I_{D6} = \frac{1}{2} k_{n6} (V_{GS6} - V_T)^2. \quad -2)$$

Similarly,

$$I_{D7} = \frac{1}{2} k_{n7} (V_{GS7} - V_T)^2 \quad -3)$$

(cont'd over)

Experiment 2.

Dividing -2) by -3) gives us:

$$\frac{I_{D6}}{I_{D7}} = \frac{k_{n6}(V_{GS6} - V_T)^2}{k_{n7}(V_{GS7} - V_T)^2} \quad - 4)$$

Now, given M_6 & M_7 are in the same branch, it must be that:

$$I_{D6} = I_{D7}$$

So we can rearrange -4) into:

$$\frac{k_{n7}}{k_{n6}} = \left[\frac{V_{GS6} - V_T}{V_{GS7} - V_T} \right]^2$$

$$\pm \sqrt{\frac{k_{n7}}{k_{n6}}} = \frac{V_{GS6} - V_T}{V_{GS7} - V_T}$$

$$\therefore \pm \sqrt{\frac{k_{n7}}{k_{n6}}} (V_{GS7} - V_T) = V_{GS6} - V_T \quad - 5)$$

Rearranging eqn -1) we see that:

$$V_{GS7} = 20 - 2V_{GS6} \quad - 6)$$

Sub -6) into -5):

$$\pm \sqrt{\frac{k_{n7}}{k_{n6}}} \cdot (20 - 2V_{GS6} - V_T) = V_{GS6} - V_T \quad - 7)$$

if we let $\pm \eta = \sqrt{\frac{k_{n7}}{k_{n6}}}$ (cont'd over)

Experiment 2

We can rewrite -7) as:

$$\pm \eta (20 - 2V_{asb} - V_T) = V_{asb} - V_T$$

Case 1

$$\eta (20 - 2V_{asb} - V_T) = V_{asb} - V_T$$

$$20\eta - 2\eta V_{asb} - \eta V_T = V_{asb} - V_T$$

$$20\eta + V_T - \eta V_T = V_{asb} + 2\eta V_{asb}$$

$$20\eta + V_T - \eta V_T = V_{asb} (1 + 2\eta)$$

$$\therefore V_{asb} = \frac{20\eta + V_T - \eta V_T}{1 + 2\eta}$$

Case 2

$$-\eta (20 - 2V_{asb} - V_T) = V_{asb} - V_T$$

$$-20\eta + 2\eta V_{asb} + \eta V_T = V_{asb} - V_T$$

$$\eta V_T - 20\eta + V_T = V_{asb} (1 - 2\eta)$$

$$\therefore V_{asb} = \frac{\eta V_T - 20\eta + V_T}{1 - 2\eta}$$

(cont'd over)

Experiment 2

Hence,

Case 1

$$V_{as6} = \frac{V_T + 20\eta - \eta V_T}{1 + 2\eta}$$

$$= \frac{V_T + \eta(20 - V_T)}{1 + 2\eta}$$

$$= \frac{2 + \sqrt{4}(20 - 2)}{1 + 2\sqrt{4}}$$

$$= \frac{2 + 2.18}{1 + 4}$$

$$= 7.6V$$

Case 2

$$V_{as6} = \frac{V_T - 20\eta + \eta V_T}{1 - 2\eta}$$

$$= \frac{V_T - \eta(20 - V_T)}{1 - 2\eta}$$

$$= \frac{2 - \sqrt{4}(20 - 2)}{1 - 2\sqrt{4}}$$

$$= \frac{2 - 2.18}{1 - 4}$$

$$= 11.33V.$$

Now, Since $V_{as7} = 20 - 2V_{as6}$

if $V_{as6} = 11.33V$, then

$$V_{as7} = 20 - 2 \cdot 11.33$$

$$\Rightarrow V_{as7} < 0$$

$$\Rightarrow V_{as7} < V_T$$

and would be in pinch off mode.

Hence, $V_{as6} = 7.6V$, $V_{as6} \neq 11.33V$

Experiment 2

Hence, if $V_{asb} = 7.6V$, then:

$$I_{D6} = I_1 = \frac{1}{2} k_{n6} (V_{asb} - V_T)^2$$


$$\therefore I_1 = \frac{1}{2} \cdot 500 \times 10^{-6} (7.6 - 2)^2$$

$$= 0.784 \text{mA}$$

Finally, $M_7 + M_8$ are identical transistors and are in the shape of a current mirror.

Hence, $I_1 = I_Q = 0.784 \text{mA}$.

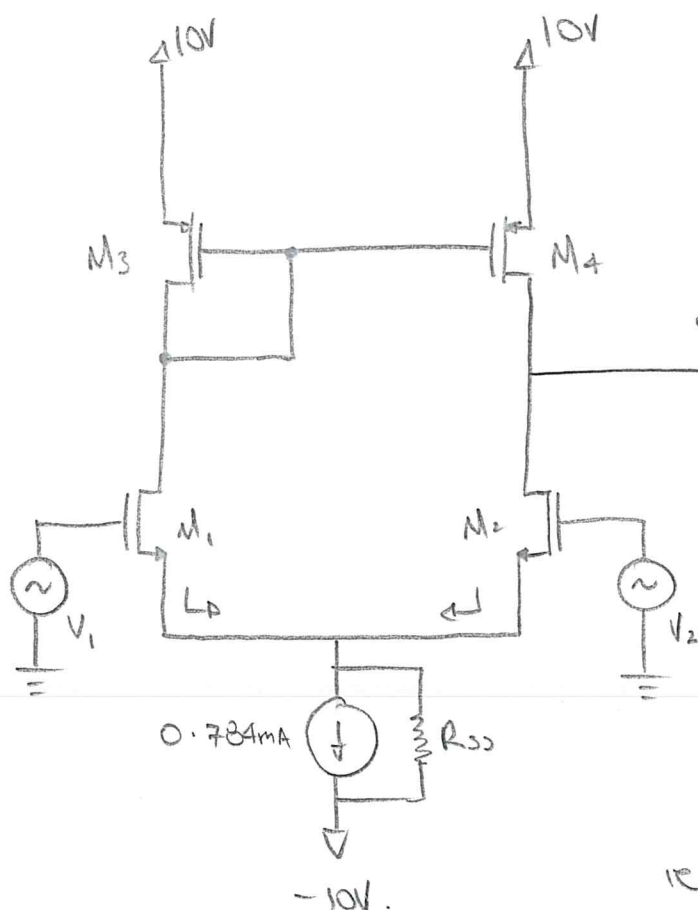Now, we turn our attention to the differential amplifier component:



We can abstract away the detail of the current source by including a constant current source in parallel with the resistor R_{SS} which represents the output resistance of the current source.


$$\text{i.e. } R_{SS} = (R_o)_{\text{current mirror}}$$

Now, we know that the finite output resistance of the current mirror is simply r_{os} .

$$\text{i.e. } R_{SS} = (R_o)_{\text{current mirror}} = r_{os}$$

Experiment 2

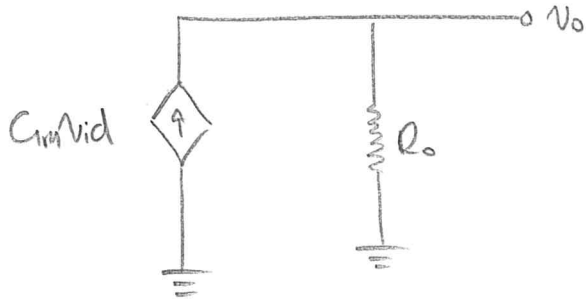Now, for a standard Differential Amp w active load we have that the general form:




where

$$R_o = r_{o2} \parallel r_{o4}$$

$$A_d = g_m (r_{o2} \parallel r_{o4})$$

$$A_{cm} = -\frac{1}{2g_{m3}R_{ss}}$$

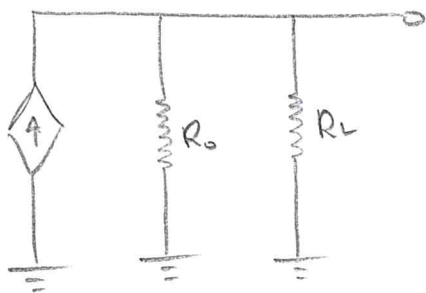But in our case we have a load at the output, R_L : Hence, our circuit looks like



Hence,

$$A_d = G_m \cdot (R_o \parallel R_L)$$

$$\therefore A_d = g_m (r_{o2} \parallel r_{o4} \parallel R_L)$$


if $r_{o2} = r_{o4}$ since transistors have identical parameters, then

$$A_d = g_m \left(\frac{1}{2} r_o \parallel R_L \right) = g_m \left(\frac{2}{r_o} + \frac{1}{R_L} \right)^{-1}$$

$$A_d = \frac{g_m r_o R_L}{2R_L + r_o}$$

Experiment 2.

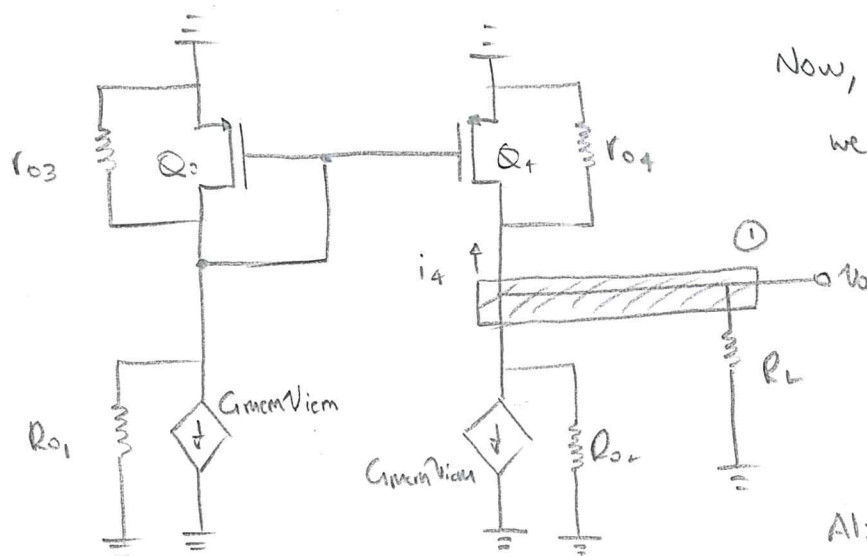Finding A_{cm} is slightly more involved. Consider the small signal model of the active loaded Diff amp



Now, from Sedra + Smith we obtain the eqⁿ for i_4 from considering the half circuit.

$$i_4 = -g_m C_{mcm} V_{cm} (R_{o1} \parallel R_{o3} \parallel \frac{1}{g_m})$$

$$\text{Also } C_{mcm} = \frac{1}{2R_{ss}}$$

By taking a node eqⁿ at ① we get that:

$$i_4 + C_{mcm} V_{cm} + \frac{V_o}{R_{o2}} + \frac{V_o}{r_{o4}} + \frac{V_o}{R_L} = 0$$

Subbing for i_4 and C_{mcm} , we get that:

$$-g_m \frac{1}{2R_{ss}} V_{cm} (R_{o1} \parallel R_{o3} \parallel \frac{1}{g_m}) + \frac{1}{2R_{ss}} V_{cm} + V_o \left(\frac{1}{R_{o2}} + \frac{1}{r_{o4}} + \frac{1}{R_L} \right) = 0.$$

$$V_o \left(\frac{1}{R_{o2}} + \frac{1}{r_{o4}} + \frac{1}{R_L} \right) = V_{cm} \frac{1}{2R_{ss}} (g_m [R_{o1} \parallel R_{o3} \parallel \frac{1}{g_m}] - 1)$$

$$\frac{V_o}{V_{cm}} = \frac{(R_{o2} \parallel r_{o4} \parallel R_L)}{2R_{ss}} (g_m [R_{o1} \parallel R_{o3} \parallel \frac{1}{g_m}] - 1)$$

$$A_{cm} = - \frac{(R_{o2} \parallel r_{o4} \parallel R_L)}{2R_{ss}} (1 - g_m [R_{o1} \parallel R_{o3} \parallel \frac{1}{g_m}])$$

(cont'd over)

Experiment 2.

Now, we just need to calculate the value of the device parameters.

$$g_m = \sqrt{2 k_n I_D}$$

$$I_{D1} = \frac{0.784 \text{ mA}}{2}$$

$$= 0.392 \text{ mA}$$

$$= \sqrt{2 \cdot 100 \text{e-6} \cdot 0.392 \text{e-3}}$$

$$k_n = 100 \mu\text{A/V}^2$$

$$= \underline{2.8 \text{e-4 S}}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.01 \cdot 0.392 \text{e-3}}$$

$$= \underline{255.1 \text{ k}\Omega}$$

$$R_{ss} = r_{os} = \frac{1}{\lambda \cdot I} = \frac{1}{0.01 \cdot 0.784 \text{e-3}}$$

$$= \underline{127.55 \text{ k}\Omega}$$

$$R_{o1} = R_{o2} = 2R_{ss} + r_o + (g_m r_o)(2R_{ss}).$$

$$= 2(127.55 \text{e3}) + 255.1 \text{e3}$$

$$+ 2.8 \text{e-4} \cdot 255.1 \text{e3} \cdot 2 \cdot 127.55 \text{e3}$$

$$= \underline{18.71 \text{ M}\Omega}$$

(cont'd over).

Experiment 2.

Now,

• If $R_L = 10\text{M}\Omega$

$$\begin{aligned} A_d &= \frac{g_m r_o R_L}{2R_L + r_o} \\ &= \frac{2.8e-4 \cdot 255.1e3 \cdot 10e6}{2 \cdot (10e6) + 255.1e3} \\ &= \underline{35.76 \frac{V}{V}} \end{aligned}$$

$$A_{cm} = -\frac{1}{2r_{o3}} (R_{o2} \parallel r_{o4} \parallel R_L) \left(1 - g_m [R_{o1} \parallel r_{o3} \parallel \frac{1}{g_m}]\right)$$

if $\frac{1}{3} = R_{o2} \parallel r_{o4} \parallel R_L$

$$\eta = R_{o1} \parallel r_{o3} \parallel \frac{1}{g_m}$$

$$\therefore A_{cm} = -\frac{1}{2r_{o3}} \cdot \frac{1}{3} \cdot (1 - g_m \eta)$$

$$\begin{aligned} \text{Now, } \frac{1}{3} &= \left(\frac{1}{18.71e6} + \frac{1}{255.1e3} + \frac{1}{10e6} \right)^{-1} \\ &= 245.5e3 \end{aligned}$$

$$\begin{aligned} \eta &= \left(\frac{1}{18.71e6} + \frac{1}{255.1e3} + 2.8e-4 \right)^{-1} \\ &= 3521.45 \end{aligned}$$

$$\begin{aligned} \therefore A_{cm} &= -\frac{1}{2 \cdot (127.55e3)} [245.5e3] (1 - 2.8e-4 \cdot 3521.45) \\ &= \underline{-0.0134 \frac{V}{V}} \end{aligned}$$

Experiment 2.

Finally, if $R_L = 400k\Omega$

$$\begin{aligned} A_d &= \frac{g_m r_o R_L}{2R_L + r_o} \\ &= \frac{2.8e-4 \cdot 255.1e3 \cdot 400e3}{2 \cdot 400e3 + 255.1e3} \\ &= \underline{27.07 \frac{V}{V}} \end{aligned}$$

$$A_{cm} = \frac{-1}{2r_{o3}} \cdot \dot{S} \cdot (1 - g_m \eta)$$

$$\text{Where } \dot{S} = R_{o2} \parallel r_{o4} \parallel R_L$$

$$\eta = R_{o1} \parallel r_{o3} \parallel \frac{1}{g_m}$$

$$\begin{aligned} \therefore \dot{S} &= \left(\frac{1}{18.71e6} + \frac{1}{255.1e3} + \frac{1}{400e3} \right)^{-1} \\ &= 154.45e3 \end{aligned}$$

$$\begin{aligned} \eta &= \left(\frac{1}{18.71e6} + \frac{1}{255.1e3} + 2.8e-4 \right)^{-1} \\ &= 3521.45. \end{aligned}$$

$$\begin{aligned} \therefore A_{cm} &= \frac{-1}{2 \cdot 127.55e3} \cdot 154.45e3 \cdot (1 - 2.8e-4 \cdot 3521.45) \\ &= \underline{-8.47e-3 \frac{V}{V}} \end{aligned}$$